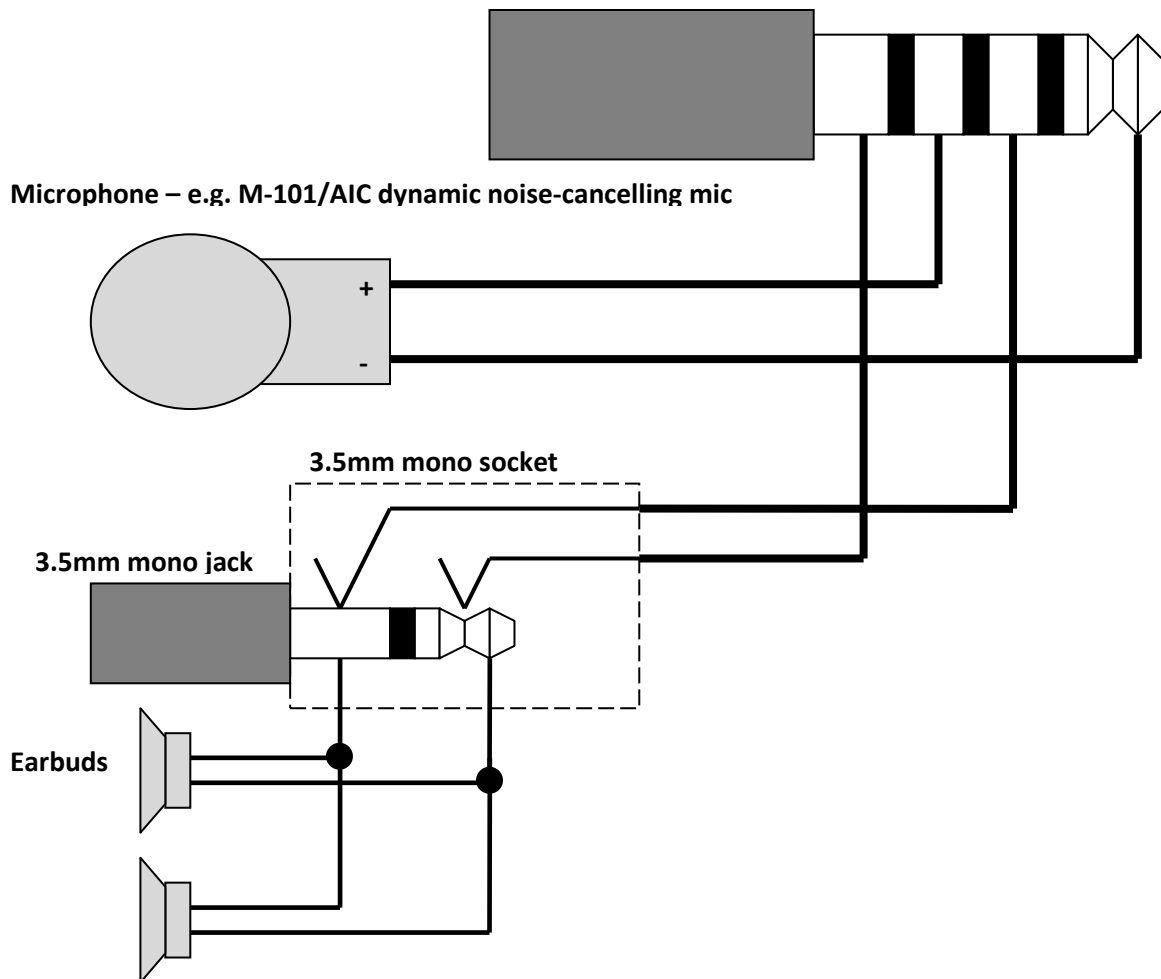


# Helmet kit

4-pin connector –Nexus TP-120, TJ120, U-174/U

Also known as 'IMSA style connector' or 'helicopter style'



This diagram shows the layout of a typical helmet kit for a race car radio system.

As always, use at your own risk, I take no responsibilities for your actions.

# Car Harness and Push-To-Talk (PTT) switch

This diagram shows the layout of a typical race car harness used with a Motorola radio.

As always, use at your own risk, I take no responsibilities for your actions.

